

Experiment Report:

Bipolar Junction Transistor Static Characteristics

Abhijnan Saraswat Gogoi
Roll no.: 2411072
PHY241 Course

3rd–4th September 2025

Abstract

An NPN transistor is connected in a circuit for common emitter configuration. The input, output and transfer characteristics of the transistor is measured by varying the currents I_C , I_B and the potential differences V_{CE} and V_{EB} accordingly. For the input characteristics, the input current I_B had an overshoot at a particular voltage V_{EB} which increased when V_{CE} was increased. In the output characteristics, the output current I_C showed a saturation after some V_{CE} for a constant I_B . The saturation current I_C increased proportionally with the input current I_B .

1 Objective

- To study the input and output characteristics of a transistor in Common Emitter mode and determine transistor parameters.

2 Theory and Working Formula

A bipolar junction, also known as a bipolar junction transistor (BJT), is a three-terminal semiconductor device that consists of two PN junctions. The three terminals are known as emitter (E), base (B) and collector (C). A BJT can be either NPN or PNP. An NPN transistor has two N-type materials on both sides of a P-type material while a PNP transistor has two P-type materials on either side of an N-type material. The working principle of the two transistors is the same but differs in the biasing of the base current and the polarity of the power supply (see figure 2). In most cases, the emitter-base junction is forward-biased whereas the collector-base junction is reverse-biased in a circuit.

A transistor can be configured in three different ways in a circuit: common emitter (CE), common base (CB) and common collector (CC). In common base (CB), the base of the transistor is connected to both the input and the output signal (preferably the ground), whereas in the common emitter (CE) and common collector (CC), the emitter and collector are connected to the common ground, respectively.

This experiment primarily studies the input, output and transfer characteristics of an NPN transistor in common emitter configuration. The circuit diagram for the experiment is given in figure 1.

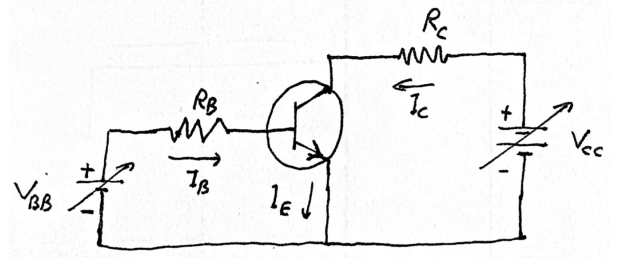


Figure 1: Circuit diagram for the experiment (common emitter configuration)

The input characteristics of the transistor is the variation of I_B as the V_{CE} (potential across the collector and emitter) is kept constant while varying I_C . The input dynamic resistance r_i is given by:

$$r_i = \frac{\Delta V_{BE}}{\Delta I_B} \quad (V_{CE} \text{ is constant}) \quad (1)$$

The output characteristics is the variation of I_E while I_B is kept constant and V_{CE} is varying. The output dynamic resistance r_o is given by:

$$r_o = \frac{\Delta V_{CE}}{\Delta I_C} \quad (I_B \text{ is constant}) \quad (2)$$

The transfer characteristics is the variation of I_C (output

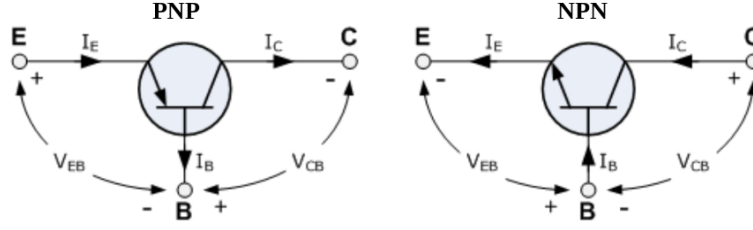


Figure 2: A schematic of an NPN bipolar junction transistor (left) and a PNP bipolar junction transistor (right)

current) with I_B (input current) for a constant V_{CE} when the transistor is active. The current amplification factor β_{dc} (for DC supply) and β_{ac} (for AC supply) is defined as follows:

$$\beta = \frac{\Delta I_C}{\Delta I_B} \quad (V_{CE} \text{ is constant}) \quad (3)$$

The value of β is usually very large, which means that a small input current I_B controls a large output current I_C . Since I_B and I_C vary proportionally, $\beta_{ac} \approx \beta_{dc}$.

3 Materials Required

(i) Bipolar junction NPN transistor (CL100 or equivalent), (ii) resistors (1k Ω , 100k Ω), (iii) breadboard, (iv) connecting wires, (v) multimeters (three quantity), (vi) DC power supply.

4 Observations

Transistor code: CDIL CL100S, Transistor type: NPN, Transistor Configuration: Common emitter (CE)
 $R_B = 100.4\text{k}\Omega$, $R_C = 0.974\text{k}\Omega$

Table 1: Input Characteristics

Sl No.	$V_{CE} = 0.061\text{V}$			$V_{CE} = 2.018\text{V}$		
	V_{EB}	V_{RB}	I_B	V_{EB}	V_{RB}	I_B
1	0.006V	0.1mV	0.0 μA	0.006V	0.1mV	0.0 μA
2	0.054V	0.5mV	0.0 μA	0.046V	0.5mV	0.0 μA
3	0.106V	1.0mV	0.01 μA	0.109V	1.0mV	0.01 μA
4	0.152V	1.4mV	0.01 μA	0.173V	1.6mV	0.02 μA
5	0.206V	1.9mV	0.02 μA	0.218V	2.0mV	0.02 μA
6	0.259V	2.4mV	0.02 μA	0.254V	2.3mV	0.02 μA
7	0.319V	3.0mV	0.03 μA	0.318V	2.9mV	0.03 μA
8	0.351V	3.6mV	0.04 μA	0.362V	3.4mV	0.03 μA
9	0.406V	7.1mV	0.07 μA	0.406V	4.2mV	0.04 μA
10	0.454V	22.6mV	0.23 μA	0.453V	7.1mV	0.07 μA
11	0.512V	162.6mV	1.62 μA	0.495V	20.5mV	0.2 μA
12	0.557V	0.823V	8.2 μA	0.537V	80.7mV	0.8 μA
13	0.575V	1.626V	16.2 μA	0.544V	106.2mV	1.06 μA
14	0.582V	2.018V	20.1 μA	0.563V	209.6mV	2.09 μA
15	0.585V	2.226V	22.17 μA	0.603V	0.981V	9.77 μA
16	0.609V	4.979V	49.59 μA	0.636V	3.644V	36.29 μA
17	0.618V	6.58V	65.54 μA	0.644V	5.257V	52.36 μA
18	0.623V	7.83V	77.99 μA	0.648V	6.360V	63.35 μA
19	0.625V	8.57V	85.36 μA	0.650V	6.920V	68.92 μA
20	0.633V	10.92V	108.76 μA	—	—	—
21	0.668V	31.70V	315.74 μA	—	—	—

Table 2: Output Characteristics

Sl. No.	$V_{R_B} = 0V$			$V_{R_B} = 1V$			$V_{R_B} = 2V$			$V_{R_B} = 3V$			$V_{R_B} = 4V$		
	V_{CE} (V)	V_{R_C}	I_C	V_{CE} (V)	V_{R_C}	I_C	V_{CE} (V)	V_{R_C}	I_C	V_{CE} (V)	V_{R_C}	I_C	V_{CE} (V)	V_{R_C}	I_C
1	0.010	0.0mV	0.0 μ A	0.006	0.0mV	0.0 μ A	0.007	0.0mV	0.0 μ A	0.006	0.0mV	0.0 μ A	0.006	0.3mV	0.3 μ A
2	0.032	0.0mV	0.0 μ A	0.029	45.1mV	46.3 μ A	0.010	10.5mV	10.8 μ A	0.016	52mV	53.4 μ A	0.017	86.6mV	88.9 μ A
3	0.979	0.0mV	0.0 μ A	0.058	184.8mV	0.190mA	0.022	60.4mV	62.0 μ A	0.025	116mV	0.119mA	0.024	159.9mV	0.164mA
4	1.652	0.1mV	0.1 μ A	0.073	310.2mV	0.318mA	0.034	130.0mV	0.134mA	0.029	162mV	0.166mA	0.031	250.5mV	0.257mA
5	1.880	0.1mV	0.1 μ A	0.090	0.520V	0.534mA	0.043	216.2mV	0.222mA	0.037	246mV	0.252mA	0.039	385.2mV	0.395mA
6	2.755	0.2mV	0.2 μ A	0.129	1.021V	1.04mA	0.052	307.2mV	0.315mA	0.044	344mV	0.353mA	0.043	0.462V	0.474mA
7	3.197	0.2mV	0.2 μ A	0.222	1.369V	1.40mA	0.060	429.8mV	0.441mA	0.050	457mV	0.470mA	0.052	0.691V	0.709mA
8	4.157	0.3mV	0.3 μ A	0.285	1.414V	1.45mA	0.067	0.541V	0.555mA	0.056	0.590V	0.606mA	0.057	0.840V	0.862mA
9	5.494	0.4mV	0.4 μ A	0.340	1.420V	1.46mA	0.072	0.655V	0.672mA	0.067	0.850V	0.872mA	0.064	1.105V	1.13mA
10	6.04	0.5mV	0.5 μ A	0.437	1.430V	1.46mA	0.081	0.846V	0.868mA	0.074	1.076V	1.10mA	0.072	1.362V	1.40mA
11	7.06	0.6mV	0.6 μ A	0.532	1.426V	1.46mA	0.090	1.068V	1.10mA	0.082	1.361V	1.40mA	0.077	1.611V	1.65mA
12	8.34	0.7mV	0.7 μ A	0.611	1.432V	1.47mA	0.097	1.258V	1.29mA	0.088	1.558V	1.60mA	0.083	1.897V	1.94mA
13	9.86	0.9mV	0.9 μ A	0.775	1.433V	1.47mA	0.103	1.422V	1.46mA	0.094	1.792V	1.84mA	0.100	2.737V	2.81mA
14	10.97	1.0mV	1.0 μ A	0.881	1.434V	1.47mA	0.111	1.650V	1.69mA	0.097	1.927V	1.98mA	0.121	3.764V	3.86mA
15	11.19	1.0mV	1.0 μ A	1.038	1.436V	1.47mA	0.118	1.820V	1.86mA	0.11	2.399V	2.46mA	0.140	4.530V	4.65mA
16	12.09	1.1mV	1.1 μ A	1.427	1.436V	1.47mA	0.133	2.139V	2.20mA	0.12	2.814V	2.88mA	0.162	5.130V	5.26mA
17	12.96	1.2mV	1.2 μ A	1.997	1.438V	1.48mA	0.144	2.342V	2.40mA	0.13	3.135V	3.22mA	0.190	5.500V	5.64mA
18	13.52	1.2mV	1.2 μ A	2.172	1.440V	1.48mA	0.163	2.584V	2.65mA	0.146	3.542V	3.64mA	0.239	5.680V	5.83mA
19	14.56	1.4mV	1.4 μ A	3.136	1.444V	1.48mA	0.176	2.678V	2.74mA	0.171	3.980V	4.08mA	0.335	5.740V	5.89mA
20	15.11	1.4mV	1.4 μ A	4.770	1.449V	1.48mA	0.216	2.798V	2.87mA	0.209	4.217V	4.32mA	0.648	5.760V	5.91mA
21	15.89	1.5mV	1.5 μ A	5.880	1.454V	1.49mA	0.330	2.856V	2.93mA	0.38	4.308V	4.42mA	0.556	5.760V	5.91mA
22	17.07	1.6mV	1.6 μ A	8.21	1.462V	1.50mA	0.450	2.870V	2.94mA	0.502	4.319V	4.43mA	0.672	5.760V	5.91mA
23	18.95	1.8mV	1.8 μ A	9.34	1.464V	1.50mA	0.562	2.873V	2.94mA	0.721	4.330V	4.44mA	0.808	5.770V	5.92mA
24	19.61	1.8mV	1.8 μ A	11.00	1.468V	1.50mA	0.800	2.875V	2.95mA	1.125	4.338V	4.45mA	1.066	5.780V	5.93mA
25	20.62	1.9mV	2.0 μ A	12.07	1.472V	1.51mA	1.019	2.879V	2.96mA	1.746	4.351V	4.46mA	1.445	5.790V	5.94mA
26	21.51	2.0mV	2.1 μ A	13.36	1.478V	1.52mA	1.289	2.883V	2.96mA	2.173	4.361V	4.48mA	1.833	5.800V	5.95mA
27	22.71	2.2mV	2.3 μ A	15.62	1.486V	1.52mA	1.607	2.888V	2.96mA	2.482	4.371V	4.48mA	2.686	5.820V	5.98mA
28	23.71	2.2mV	2.3 μ A	18.98	1.496V	1.54mA	1.930	2.892V	2.96mA	3.228	4.385V	4.50mA	2.994	5.830V	5.98mA
29	25.34	2.4mV	2.5 μ A	20.86	1.505V	1.54mA	2.891	2.901V	2.98mA	6.58	4.440V	4.56mA	3.170	5.860V	6.02mA
30	27.14	2.6mV	2.7 μ A	24.79	1.521V	1.56mA	3.704	2.911V	2.98mA	7.35	4.460V	4.58mA	3.640	5.880V	6.04mA
31	-	-	-	28.50	1.531V	1.57mA	4.691	2.921V	3.00mA	10.64	4.520V	4.64mA	4.169	5.900V	6.06mA
32	-	-	-	-	-	-	7.16	2.953V	3.03mA	13.28	4.570V	4.69mA	4.452	5.900V	6.06mA
33	-	-	-	-	-	-	-	-	-	-	-	-	9.72	6.100V	6.26mA
34	-	-	-	-	-	-	-	-	-	-	-	-	12.30	6.170V	6.33mA

Table 3: Transfer Characteristics for $V_{CE} \approx 1.8V$

Sl. No.	V_{R_B} (in V)	I_B (in μA)	I_C (in mA)
1	0.0	0.00	0.00
2	1.0	9.96	1.48
3	2.0	19.92	2.96
4	3.0	29.88	4.46
5	4.0	39.84	5.95

5 Results

The values of the current I_B in table 1 are calculated from the V_{R_B} column and the measured resistance R_B upto the correct significant figures. Similarly, for table 2, I_C is determined from the respective V_{R_C} and the measured resistance R_C . Instead of an ammeter, a voltmeter is used to measure the voltage drop across the resistors R_C and R_B to obtain the currents I_C and I_B respectively. Similarly in table 3, the I_B is calculated from V_{R_B} and the resistance R_B . The graph plots of the data in tables 1, 2 and 3 are given in figure 3.

To obtain the input dynamic resistance of the transistor, the data points with $V_{EB} \leq 0.62$ were excluded for $V_{CE} = 0.061V$ and $V_{CE} = 2.018V$. Then, individually for each V_{CE} , linear fit was performed to obtain the slope of the V_{EB} v/s I_B plot which corresponds with the input dynamic resistance r_i for that V_{CE} . The results for r_i are as follows:

Table 4: Input dynamic resistance r_i obtained for two different V_{CE}

V_{CE} (in V)	r_i (in Ω)
0.061	1.8 ± 0.1
2.018	4.3 ± 0.2

For the output dynamic resistance of the transistor, the data for $V_{CE} \leq 0.5V$ in table 2 were excluded and a linear fit was performed for each I_B current for the I_C v/s V_{CE} plot (see figure 3). The slope of the line of best-fit is r_o for the given I_B current. The values of r_o obtained are as follows:

Table 5: Output dynamic resistance r_o obtained for different input currents I_B

I_B (in μA)	r_o (in $k\Omega$)
0.00	9735.5 ± 86.5
9.96	273.0 ± 4.1
19.92	81.6 ± 1.5
29.88	50.8 ± 0.8
39.84	26.9 ± 0.5

To determine the current amplification factor β_{dc} , a linear fit was performed on the data of table 3, where the slope of the I_C v/s I_B graph is β_{ac} obtained as:

$$\beta_{ac} = 149.4 \pm 0.2$$

6 Discussion

The graph plots of the input, output and transfer characteristics are given in figure 3. The input characteristics show a large increase in the I_B after a threshold V_{EB} voltage. Also, this threshold V_{EB} seems to increase with the V_{CE} by comparing the plots for $V_{CE} = 0.061V$ and $V_{CE} = 2.018V$. This may intuitively make sense as $I_C + I_B = I_E$ and an increase in V_{CE} facilitates an increase in I_C which may compensate for the shift of the graph.

In the plot of the output characteristics, the output current I_C reaches a saturation after some V_{CE} which is consistent with the theory. Also, this saturation current of I_C increases with the increase in the input current I_B which shows the application of an NPN transistor a device to ‘scale-up’ or ‘scale-down’ the amplitude of a given signal. Also, this current amplification can be more clearly studied from the plot for transfer characteristics (see figure 3) which shows a linear relationship between the input current I_B and the output current I_C . This result is also consistent with the theory.

It can be observed from table 5 that the output dynamic resistance of the transistor decreases with the increase in the input base current I_B . Also, the value of the current amplification factor β_{ac} is a very large value which indicates that a very small input base current (a few μA) can control the flow of a large current (in mA) I_C which is consistent with the theory.

7 Conclusion

The input and output characteristics of the NPN transistor in common emitter configuration has been studied successfully and the values of its input dynamic resistance, output dynamic resistance and the current amplification factor are obtained.

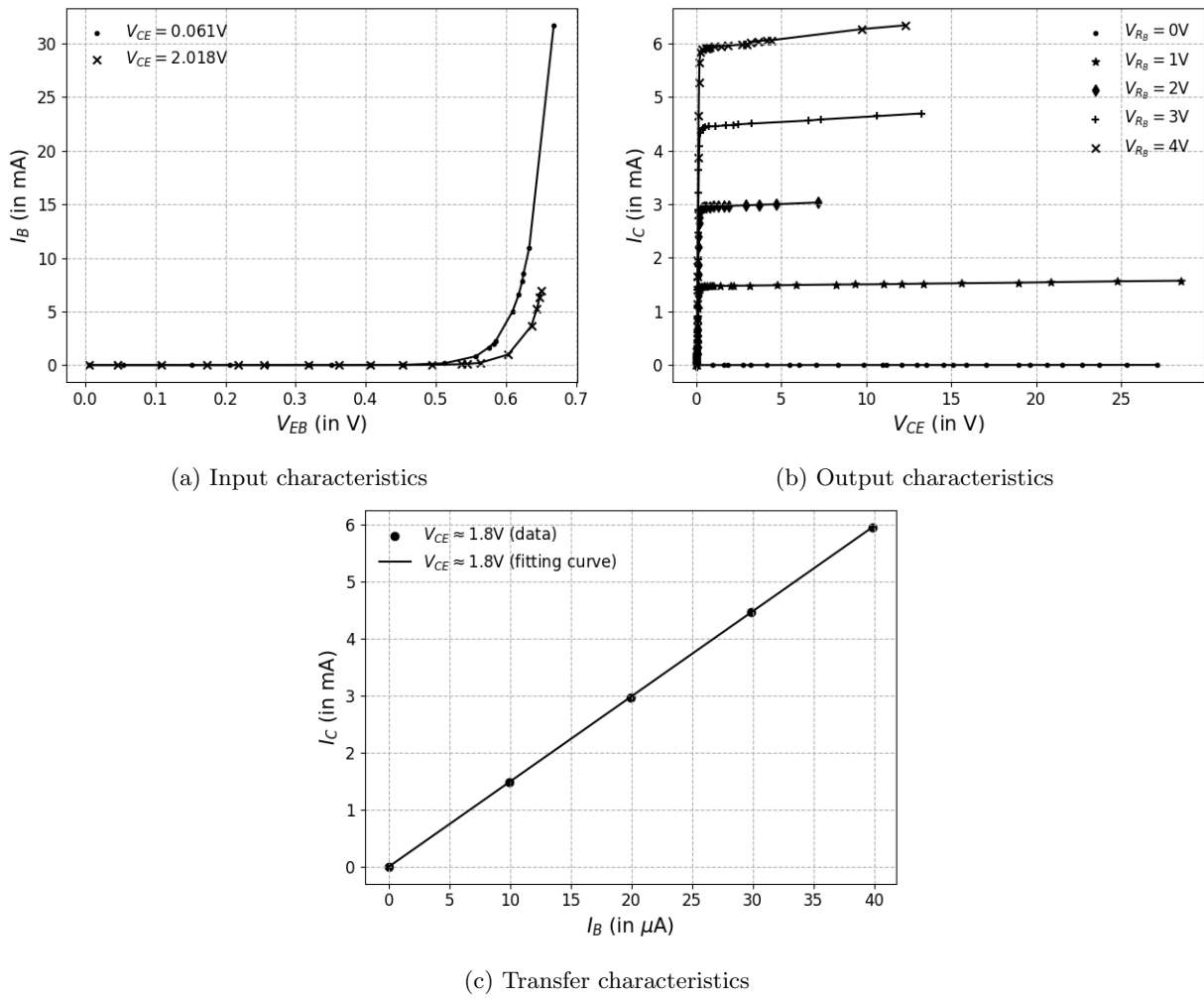


Figure 3: Plots of the experiment from the observation tables 1, 2 and 3.

8 Precautions

1. Ensure that the three terminals of the NPN transistor are correctly identified and connected in the circuit.
2. The ground of the two voltage sources must be shorted in the circuit.